

ECE 448: Quiz 2 Solutions

For the given below circuit implementing sorting of four n-bit numbers, determine values of all control signals listed in the table during the execution of the instructions listed in the first column of the table.



