

Lecture 5


Conditional-Sum Adder

Hybrid Adders

Parallel Prefix Network Adders

Carry-Select Adders

One-level k-bit Carry-Select Adder

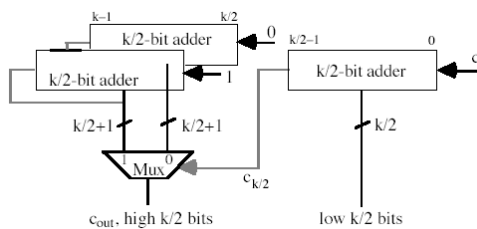


One-level k-bit Carry-Select Adder
Cost & Latency

$$C_{\text{select-add}}(k) = 3C_{\text{add}}(k/2) + k/2 + 1$$


$$T_{\text{select-add}}(k) = T_{\text{add}}(k/2) + 1$$

Two-level k-bit Carry Select Adder

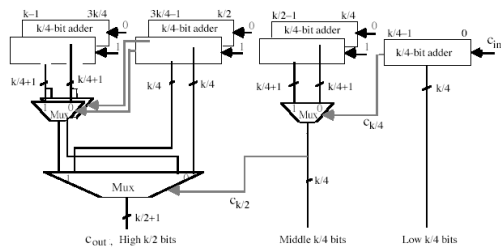

Conditional-Sum Adder

Top-level Block of Conditional-Sum Adder

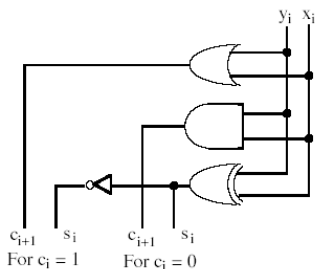

Operation of a 16-bit Conditional-Sum Adder

Block width	Block carry in	s	c	Block sum and block carry-out																c _{out}
				15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	
1	0	s	c	0	0	1	0	0	1	1	0	1	1	1	0	1	1	0	1	0
	1	s	c	0	1	0	1	0	1	1	0	1	1	1	0	1	1	0	1	0
2	0	s	c	0	1	0	1	0	1	1	0	1	1	0	1	1	0	1	0	
	1	s	c	0	1	0	1	0	1	1	0	1	1	0	1	1	0	1	0	
4	0	s	c	0	1	1	0	0	0	1	0	0	1	1	0	1	1	1	1	
	1	s	c	0	1	1	0	0	1	0	1	0	0	1	1	0	0	1	1	
8	0	s	c	0	1	1	0	0	0	1	0	1	0	0	0	1	1	1	1	
	1	s	c	0	1	1	0	0	1	0	1	0	0	1	0	0	1	1	1	
16	0	s	c	0	1	1	0	0	1	0	0	1	0	0	0	1	1	1	1	
	1	s	c	0	1	1	0	0	1	0	0	1	0	0	0	1	1	1	1	

Conditional-Sum Adder

Multilevel carry-select idea carried out to the extreme, until we arrive at single-bit blocks.

$$C(k) \approx 2C(k/2) + k + 2 \approx k (\log_2 k + 2) + k C(1)$$


$$T(k) = T(k/2) + 1 = \log_2 k + T(1)$$

where C(1) and T(1) are the cost and delay of the circuit of Fig. 7.11 used at the top to derive the sum and carry bits with a carry-in of 0 and 1


The term k + 2 in the first recurrence represents an upper bound on the number of single-bit 2-to-1 multiplexers needed for combining two k/2-bit adders into a k-bit adder

Hybrid Adders

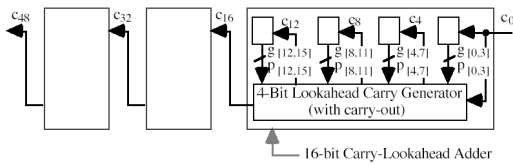A Hybrid Ripple-Carry/Carry-Lookahead Adder



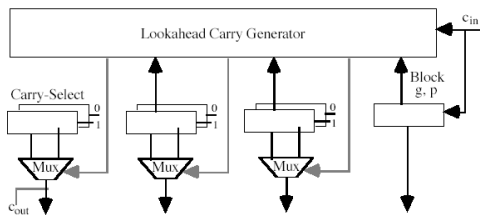
A Hybrid Carry-Lookahead/Carry-Select Adder



Parallel Prefix Network Adders

Parallel Prefix Network Adders

Basic component - Carry operator (1)

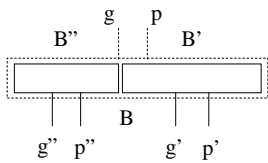


$$g = g'' + g'p''$$

$$p = p'p''$$

$$(g, p) = (g', p') \ell (g'', p'') = (g'' + g'p'', p'p'')$$

Parallel Prefix Network Adders

Basic component - Carry operator (2)

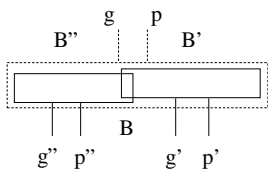

$$g = g'' + g'p''$$

$$p = p'p''$$

$$(g, p) = (g', p') \ell (g'', p'') = (g'' + g'p'', p'p'')$$

Properties of the carry operator ζ

Associative

$$[(g_1, p_1) \zeta (g_2, p_2)] \zeta (g_3, p_3) = (g_1, p_1) \zeta [(g_2, p_2) \zeta (g_3, p_3)]$$

Not commutative

$$(g_1, p_1) \zeta (g_2, p_2) \neq (g_2, p_2) \zeta (g_1, p_1)$$

Parallel Prefix Network Adders

Major concept

Given:

$$(g_0, p_0) \quad (g_1, p_1) \quad (g_2, p_2) \quad \dots \quad (g_{k-1}, p_{k-1})$$

Find:

$$(g_{[0,0]}, p_{[0,0]}) (g_{[0,1]}, p_{[0,1]}) (g_{[0,2]}, p_{[0,2]}) \dots (g_{[0,k-1]}, p_{[0,k-1]})$$

$$c_i = g_{[0,i-1]} + c_0 p_{[0,i-1]}$$

Parallel Prefix Network Adders

Similar problem

Parallel Prefix Sum Problem

Given:

$$x_0 \quad x_1 \quad x_2 \quad \dots \quad x_{k-1}$$

Find:

$$x_0 \quad x_0 + x_1 \quad x_0 + x_1 + x_2 \quad \dots \quad x_0 + x_1 + x_2 + \dots + x_{k-1}$$

Parallel Prefix Adder Problem


Given:

$$x_0 \quad x_1 \quad x_2 \quad \dots \quad x_{k-1}$$

Find:

$$x_0 \quad x_0 \zeta x_1 \quad x_0 \zeta x_1 \zeta x_2 \quad \dots \quad x_0 \zeta x_1 \zeta x_2 \zeta \dots \zeta x_{k-1}$$

$$\text{where } x_i = (g_i, p_i)$$

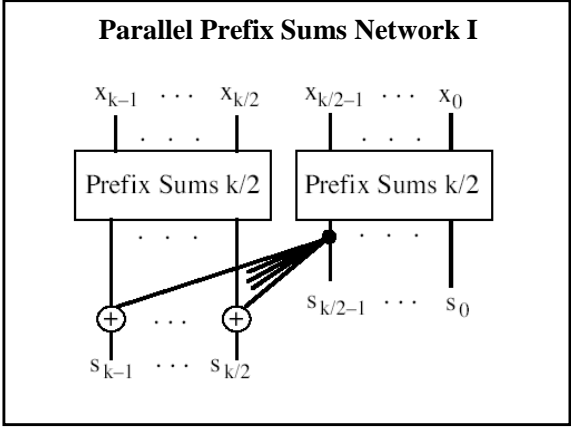

Parallel Prefix Sums Network I
Cost Analysis


Cost = C(k) = 2 C(k/2) + k/2 =
 $= 2 [2C(k/4) + k/4] + k/2 = 4 C(k/4) + k/2 + k/2 =$
 $= \dots =$
 $= 2^{\log_2 k - 1} C(2) + k/2 (\log_2 k - 1) =$
 $= k/2 \log_2 k$ $\left| C(2) = 1 \right|$

Example:
 $C(16) = 2 C(8) + 8 = 2[2 C(4) + 4] + 8 =$
 $= 4 C(4) + 16 = 4 [2 C(2) + 2] + 16 =$
 $= 8 C(2) + 24 = 8 + 24 = 32 = (16/2) \log_2 16$

Parallel Prefix Sums Network I
Delay Analysis

Delay = D(k) = D(k/2) + 1 =
 $= [D(k/4) + 1] + 1 = D(k/4) + 1 + 1 =$
 $= \dots =$
 $= \log_2 k$ $\left| D(2) = 1 \right|$

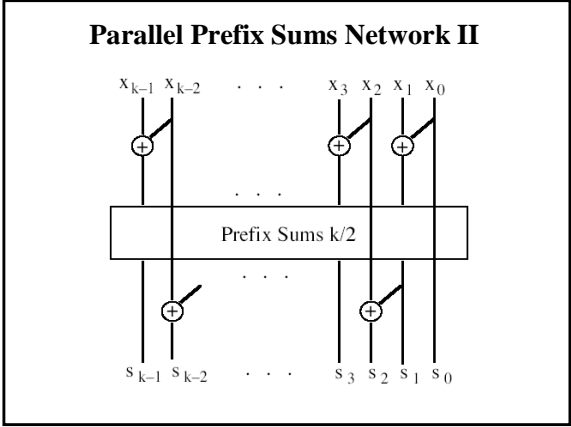Example:
 $D(16) = D(8) + 1 = [D(4) + 1] + 1 =$
 $= D(4) + 2 = [D(2) + 1] + 2 =$
 $= 4 = \log_2 16$



Parallel Prefix Sums Network II
Cost Analysis

Cost = C(k) = C(k/2) + k - 1 =
 $= [C(k/4) + k/2 - 1] + k - 1 = C(k/4) + 3k/2 - 2 =$
 $= \dots =$
 $= C(2) + (2k - 2k/2^{\log_2 k - 1}) - (\log_2 k - 1) =$
 $= 2k - 2 - \log_2 k$ $\left| C(2) = 1 \right|$


Example:
C(16) = C(8) + 16 - 1 = [C(4) + 8 - 1] + 16 - 1 =
 $= C(2) + 4 - 1 + 24 - 2 = 1 + 28 - 3 = 26$
 $= 2 \cdot 16 - 2 - \log_2 16$

Parallel Prefix Sums Network II
Delay Analysis


Delay = D(k) = D(k/2) + 2 =
 $= [D(k/4) + 2] + 2 = D(k/4) + 2 + 2 =$
 $= \dots =$
 $= 2 \log_2 k - 1$ $\left| D(2) = 1 \right|$

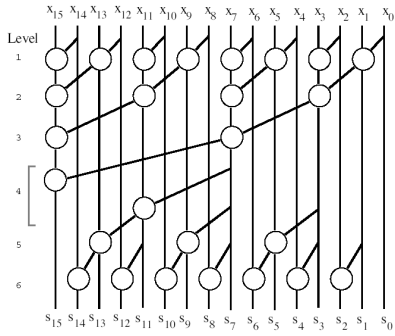Example:
D(16) = D(8) + 2 = [D(4) + 2] + 2 =
 $= D(4) + 4 = [D(2) + 2] + 4 =$
 $= 7 = 2 \log_2 16 - 1$

Brent-Kung parallel prefix graph for 16 inputs



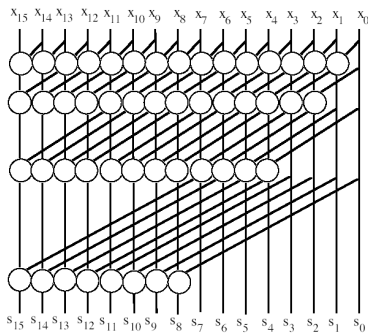Kogge-Stone parallel prefix graph for 16 inputs




Parallel Prefix Network Adders

Comparison of architectures

	Network 2 Brent-Kung	Hybrid	Kogge-Stone
Delay(k)	$2 \log_2 k - 2$	$\log_2 k + 1$	$\log_2 k$
Cost(k)	$2k - 2 - \log_2 k$	$k/2 \log_2 k$	$k \log_2 k - k + 1$
Delay(16)	6	5	4
Cost(16)	26	32	49
Delay(32)	8	6	5
Cost(32)	57	80	129

Latency-Cost Trade-off

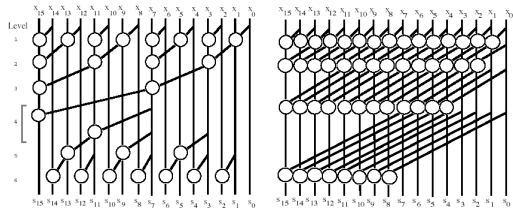

B-K: Six levels, 26 cells K-S: Four levels, 49 cells

A Hybrid Brent-Kung/Kogge-Stone parallel prefix graph for 16 inputs

Hybrid: Five levels, 32 cells

